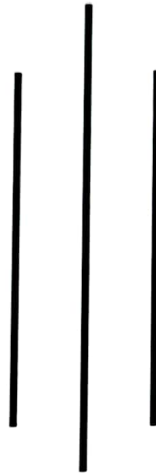


TRIBHUVAN UNIVERSITY

# PATAN MULTIPLE CAMPUS

PATAN DHOKA, LALITPUR



DIGITAL LOGIC (BIT 103)

LAB ...7...

SUBMITTED BY

SUBMITTED TO

NAME: Suresh Dahal

CLASS: BIT - I-I

ROLL NO: 23

DATE: 2080/12/16

JYOTI PRAKASH CHAUDHARY

.....  
  
CHECKED BY

TITLE:- DESIGN SEVEN SEGMENT DISPLAY CIRCUIT TO DISPLAY THE DECIMAL NUMBERS 1, 7 AND 3.

9.) OBJECTIVE:-

→ To design seven segment display circuit to display the decimal numbers 1, 7 and 3

6.) REQUIREMENTS:-

- i) Digital Logic kit and Simulator
- ii) Logic gates and connecting wires
- iii) Interactive / sequence generator as input
- iv) 7 segment display as output
- ~~v) LED~~

C.) THEORY:-

Seven segment display consists of 7 segments a, b, c, d, e, f, g to display numbers or characters. BCD input is given to the BCD to 7 segment decoder which gives (7) seven outputs.

TRUTH TABLE

Inputs				Outputs						
A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	0	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

# LOGIC EXPRESSION

For a

AB \ CD	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	1		1	1
$\bar{A}B$		1	1	1
$AB$	X	X	X	X
$A\bar{B}$	1	1	X	X

$$a = A + C + B'D' + BD$$

For b

AB \ CD	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	1	1	1	1
$\bar{A}B$	1		1	
$AB$	X	X	X	X
$A\bar{B}$	1	1	X	X

$$b = B' + CD + C'D'$$

For c

AB \ CD	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	1	1	1	
$\bar{A}B$	1	1	1	1
$AB$	X	X	X	X
$A\bar{B}$	1	1	X	X

$$c = C' + D + B$$

For d

AB \ CD	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	$CD$
$\bar{A}\bar{B}$	1		1	1
$\bar{A}B$		1		1
$A\bar{B}$	x	x	x	x
$AB$	1	1	x	x

$$d = B'D' + A + \bar{B}C + BC'D + CD'$$


For g

AB \ CD	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	$CD$
$\bar{A}\bar{B}$			1	1
$\bar{A}B$	1	1		1
$A\bar{B}$	x	x	x	x
$AB$	1	1	x	x


$$g = A + B\bar{C} + \bar{C}\bar{D} + \bar{B}C$$

## LOGIC CIRCUITS


To display 1

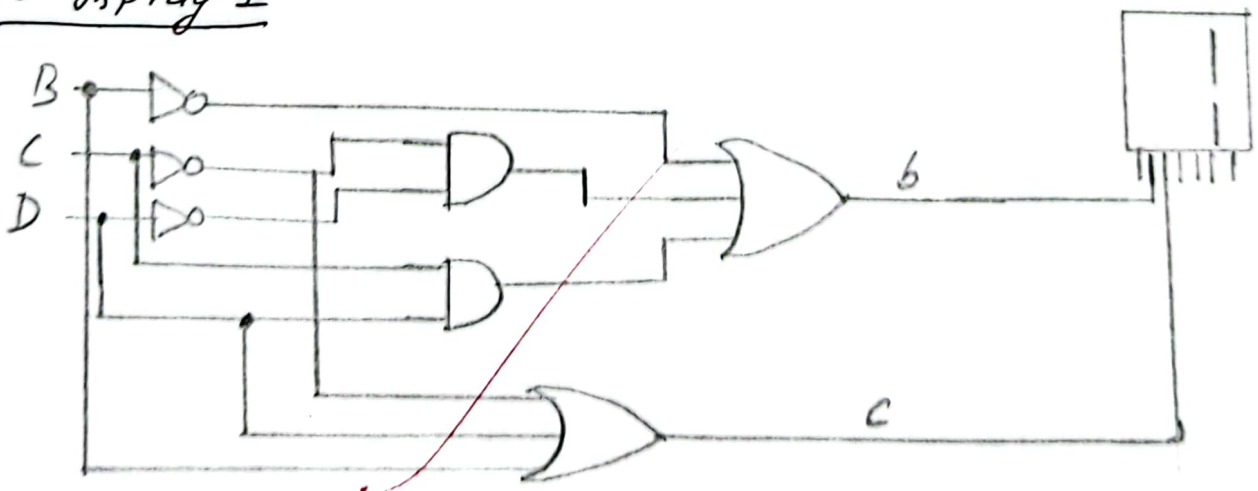

To display 7

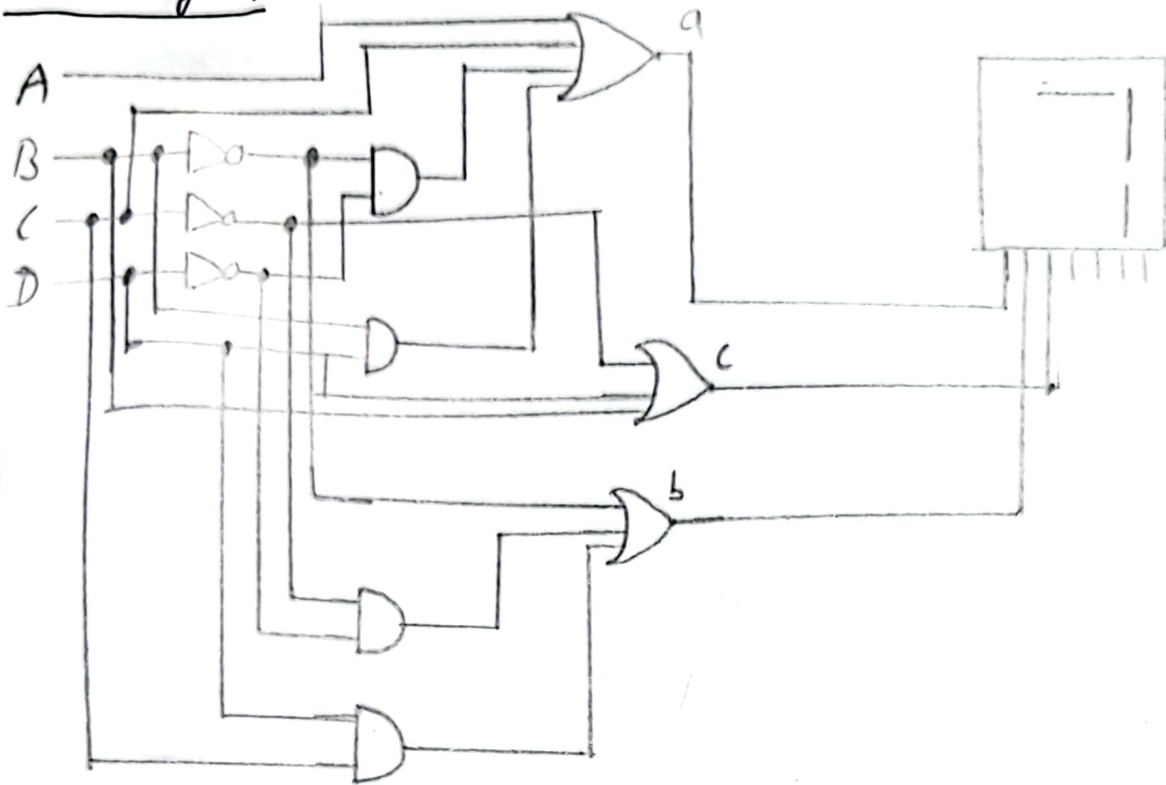

To display 3

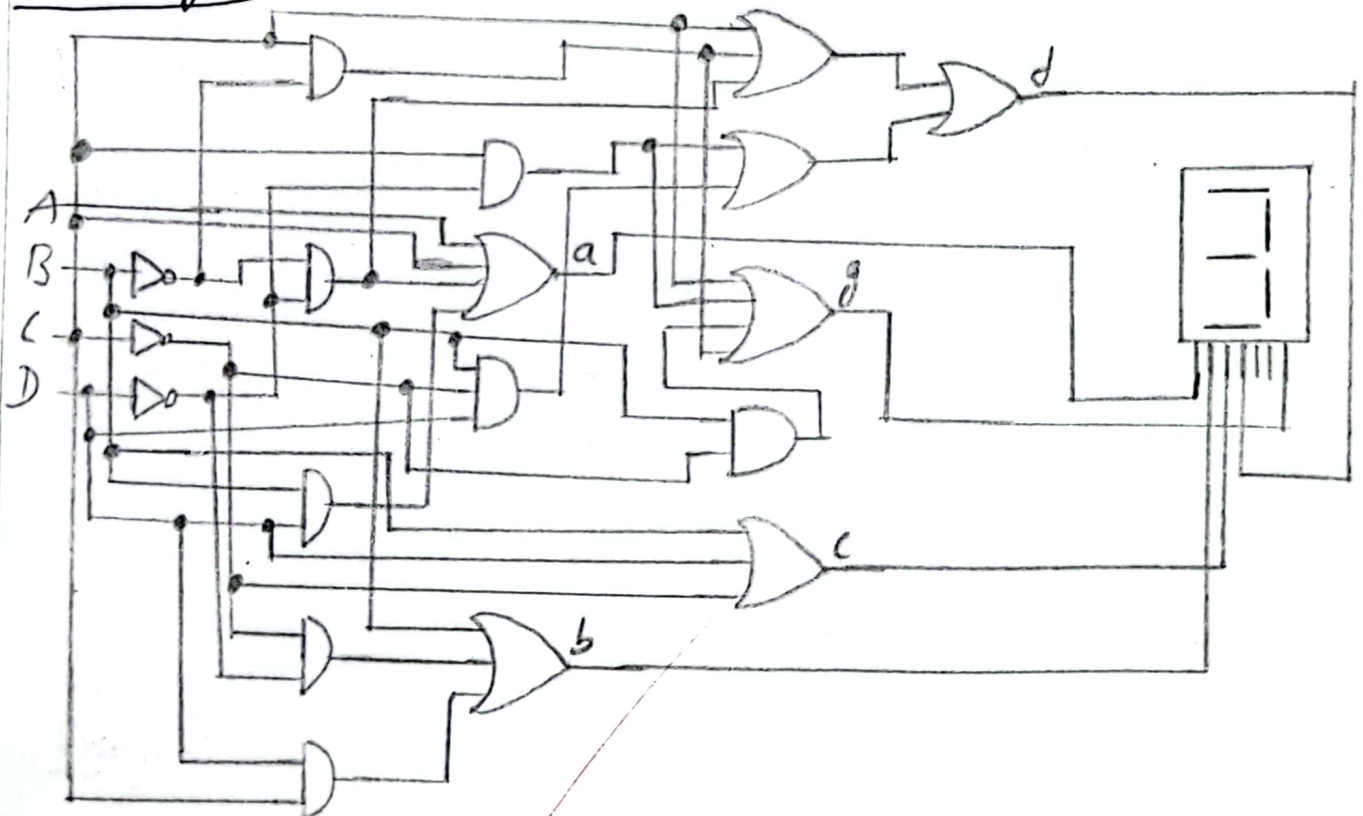

d) CONCLUSION:-

In this lab we have designed the seven segment display using different gates to display the numbers 1, 3 and 7.

*[Handwritten signature]*