 


TRIBHUVAN UNIVERSITY

PATAN MULTIPLE CAMPUS

PATAN DHOKA, LALITPUR



DIGITAL LOGIC (BIT 103)

LAB *9*...

SUBMITTED BY

NAME: *Suresh Datta*


CLASS: *B.T. - I/II*

ROLL NO: *23*

DATE: *20.8.01/21/26*

SUBMITTED TO

JYOTI PRAKASH CHAUDHARY

.....

CHECKED BY

TITLE:- REALIZE MASTER SLAVE FLIP-FLOP CIRCUIT WITH LOGIC DIAGRAM, TRUTH TABLE AND TIMING DIAGRAM

a) OBJECTIVE

→ To realize master-slave flip-flop circuit with logic diagram, truth table and timing diagram

b) REQUIREMENTS


- i) Digital Logic kit and Simulator
- ii) 8 NAND gates, 1 NOT gate
- iii) Connecting wires
- iv) Interactive / sequence generator as input
- v) LED as output

c) THEORY

1.) INTRODUCTION

It consists of two flip-flops. one is called master and another is called slave. Output from master is given input for slave and clock pulse provided to each flip-flop is complement of each other.


2.) LOGIC DIAGRAM

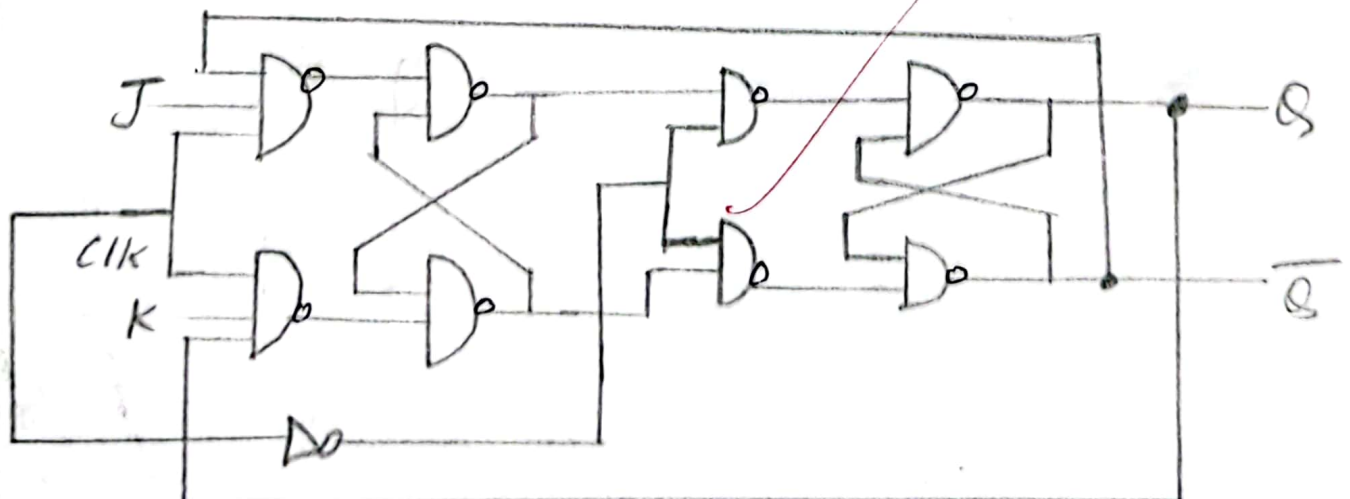

3. CHARACTERISTIC TABLE

inputs			outputs		Remark
clk	J	K	Q_{n+1}	\overline{Q}_{n+1}	
x	0	0	Q_n	\overline{Q}_n	No change
↑	0	0	Q_n	\overline{Q}_n	No change
↑	0	1	0	1	Reset
↑	1	0	1	0	Set
↑	1	1	\overline{Q}_n	Q_n	Toggle

4. TIMING DIAGRAM:-

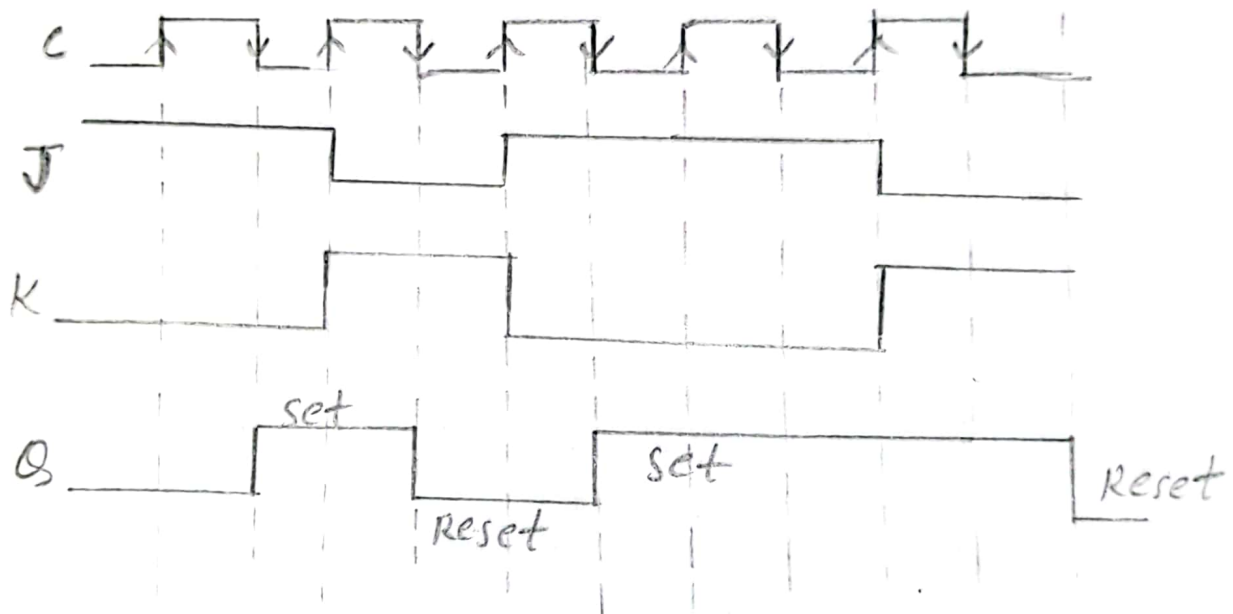

5. CONCLUSION:-

In this lab, we have realized master slave flip flop with logic diagram, truth table and timing diagram.

[Handwritten signature]