

Unit 6

Counters and Registers

Introduction

Circuits that include flip-flops are usually classified by the **function** they perform. Two such circuits are counters and registers.

Counters

- A register that goes through a predetermined sequence of states upon the application of input pulses
- The gates in a counter are connected in such a way as to produce a predefined sequence of binary states in the register.

Registers

- ❖ A group of binary cells (FFs) suitable for holding binary data information

- ❖ In addition to the FFs, a register may have combinational gates to control when and how the new information is transferred into the register

Counters

- **Counters** are circuits that cycle through a specified number of states.

Two types of counters:

- ❖ Asynchronous (ripple) counters
 - ❖ Synchronous (parallel) counters
- **Ripple counters** allow some flip-flop outputs to be used as a source of clock for other flip-flops.

- **Synchronous counters** apply the same clock to all flip flops.

Asynchronous Vs synchronous Counters

| Sr. No. | Asynchronous Counters | Synchronous Counters |
|---------|--|--|
| 1. | In this type of counter flip-flops are connected in such a way that output of first flip-flop drives the clock for the next flip-flop. | In this type there is no connection between output of first flip-flop and clock input of the next flip-flop. |
| 2. | All the flip-flops are not clocked simultaneously. | All the flip-flops are clocked simultaneously. |
| 3. | Logic circuit is very simple even for more number of states. | Design involves complex logic circuit as number of states increases. |
| 4. | Main drawback of these counters is their low speed as the clock is propagated through number of flip-flops before it reaches last flip-flop. | As clock is simultaneously given to all flip-flops there is no problem of propagation delay. Hence they are preferred when number of flip-flops increases in the given design. |

Asynchronous (Ripple) Counters



Asynchronous counters: The flip-flops **do not change states at exactly the same time** as they do not have a common clock pulse.

- Also known as **ripple counters**, as the input clock pulse “ripples” through the counter – cumulative delay is a drawback.
- n flip-flops: a MOD (modulus) 2^n counter. (Note: A MOD- x counter cycles through x states.)
- Output of the last flip-flop (MSB) divides **the input clock frequency by the MOD number of the counter**, hence a counter is also a *frequency divider*.

- Idea:
 - to connect the output of one flip-flop to the C input of the next high-order flip-flop
- We need “complementing” flip-flops – We can use T flip-flops to obtain complementing flip flops or
 - JK flip-flops with its inputs are tied together

2 bit Ripple binary up Counters

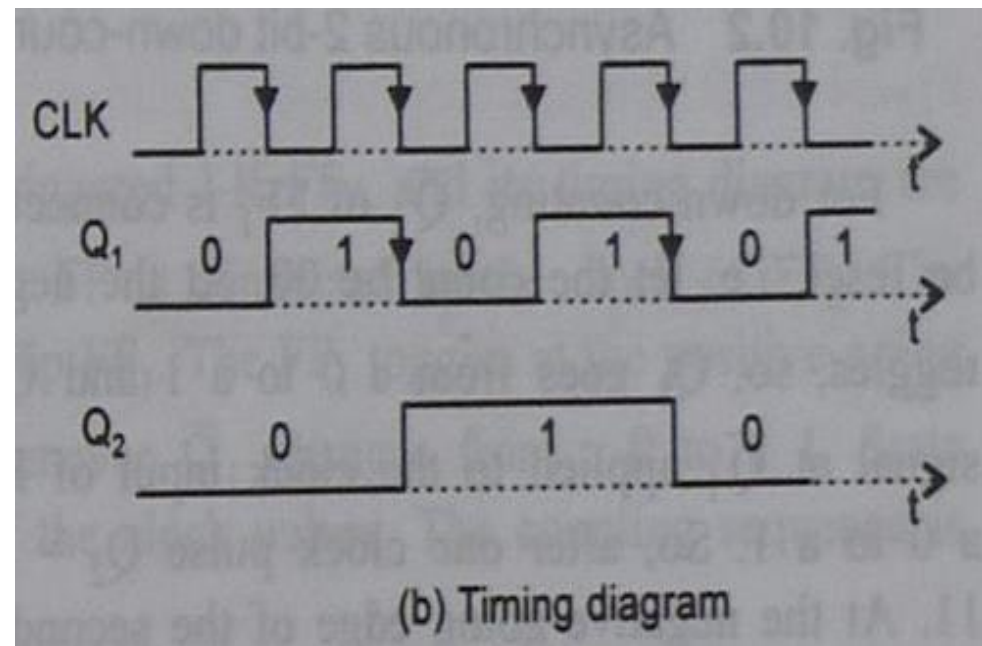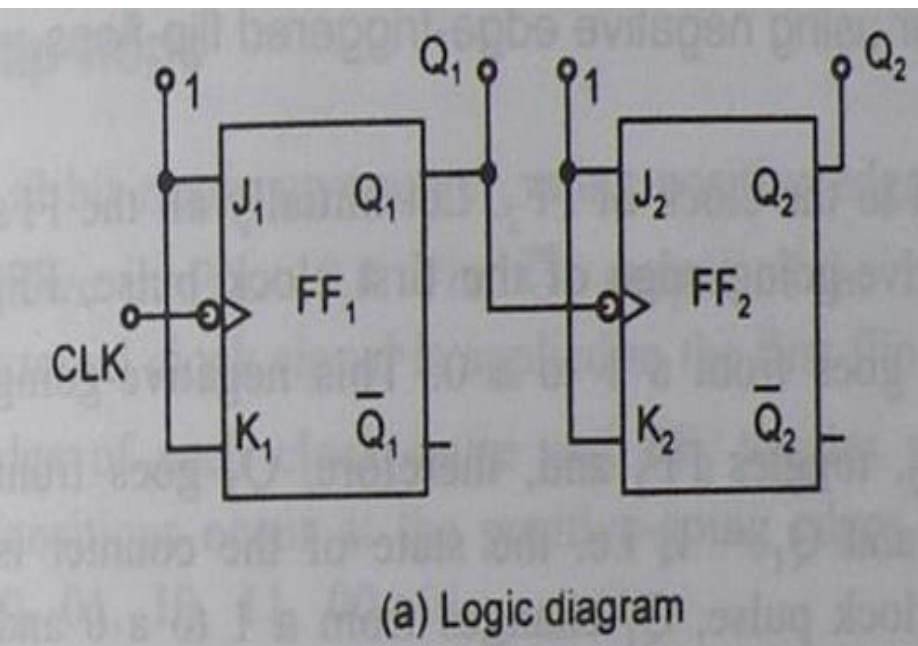- Output of one flip-flop is connected to the clock input of the next more-significant flip-flop.



Timing diagram

Count Sequence

Q2 Q1

0 0

0 1


1 0


1 1

0 0 ...

Asynchronous (Ripple) Counters

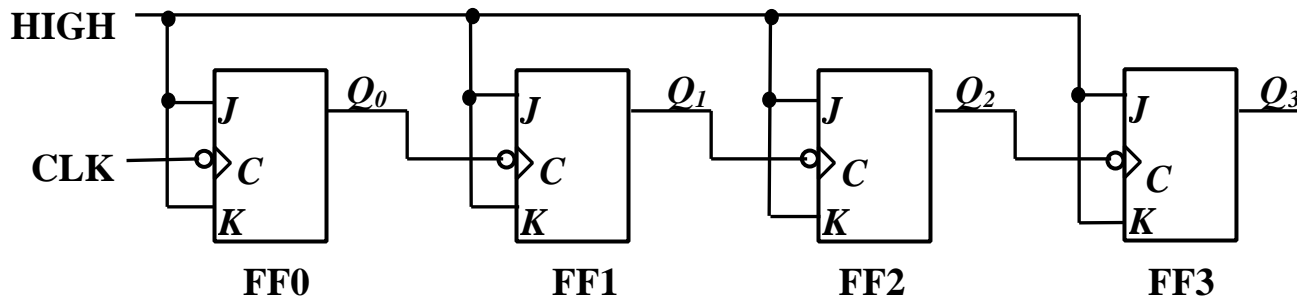- **Example: 4-bit ripple binary counter** (negative edge triggered).



 

Binary Ripple Counter

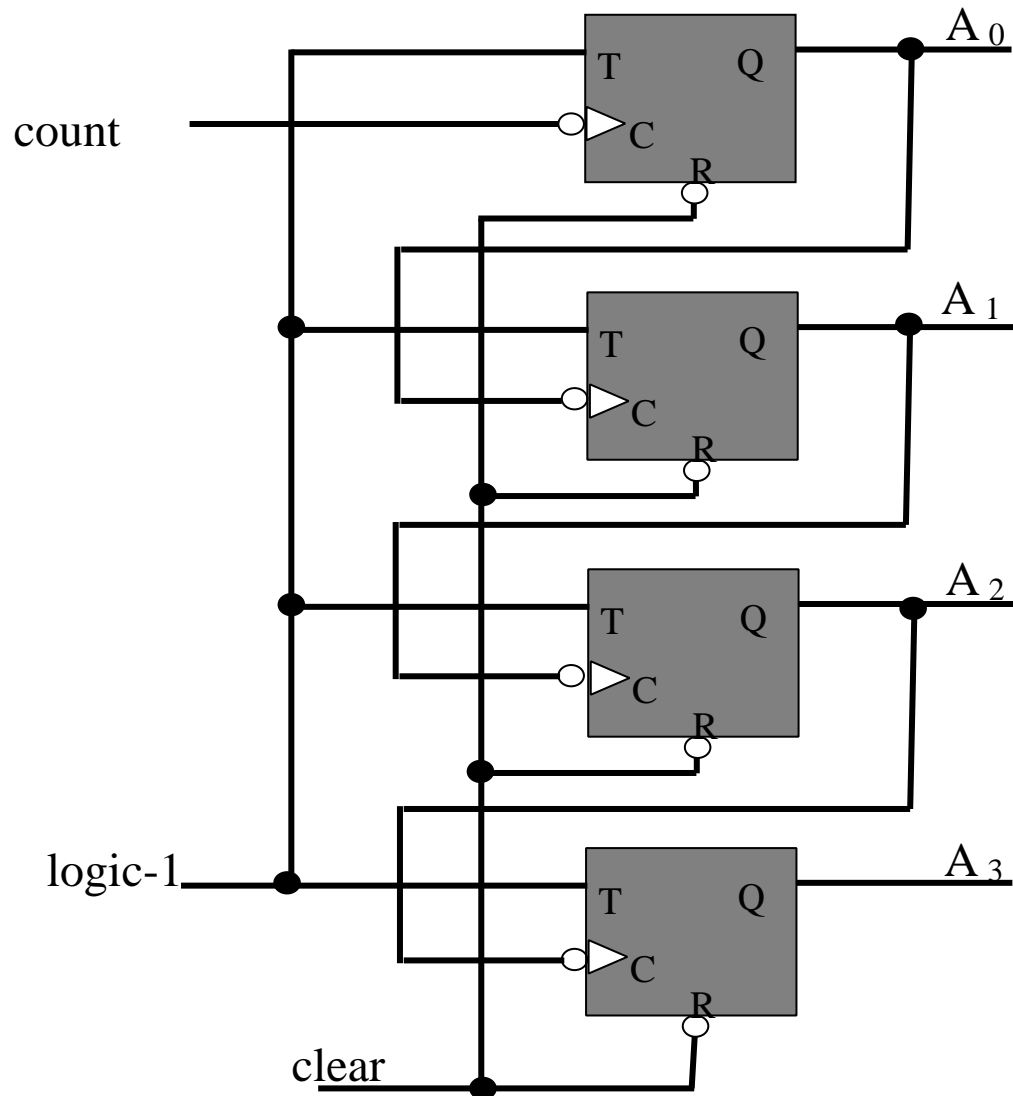


Fig: 4-bit Binary Ripple Counter

| | A ₃ | A ₂ | A ₁ | A ₀ |
|----|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 2 | 0 | 0 | 1 | 0 |
| 3 | 0 | 0 | 1 | 1 |
| 4 | 0 | 1 | 0 | 0 |
| 5 | 0 | 1 | 0 | 1 |
| 6 | 0 | 1 | 1 | 0 |
| 7 | 0 | 1 | 1 | 1 |
| 8 | 1 | 0 | 0 | 0 |
| 9 | 1 | 0 | 0 | 1 |
| 10 | 1 | 0 | 1 | 0 |
| 11 | 1 | 0 | 1 | 1 |
| 12 | 1 | 1 | 0 | 0 |
| 13 | 1 | 1 | 0 | 1 |
| 14 | 1 | 1 | 1 | 0 |
| 15 | 1 | 1 | 1 | 1 |

Fig: Count Sequence

Operation

- It is obvious that the lowest-order bit A_0 must be complemented with each count pulse.
- Every time A_0 goes from 1 to 0, it complements A_1 .
- Every time A_1 goes from 1 to 0, it complements A_2 .
- Every time A_2 goes from 1 to 0, it complements A_3 , and so on.
- The flip-flops change one at a time in rapid succession, and the signal propagates through the counter in a ripple fashion.

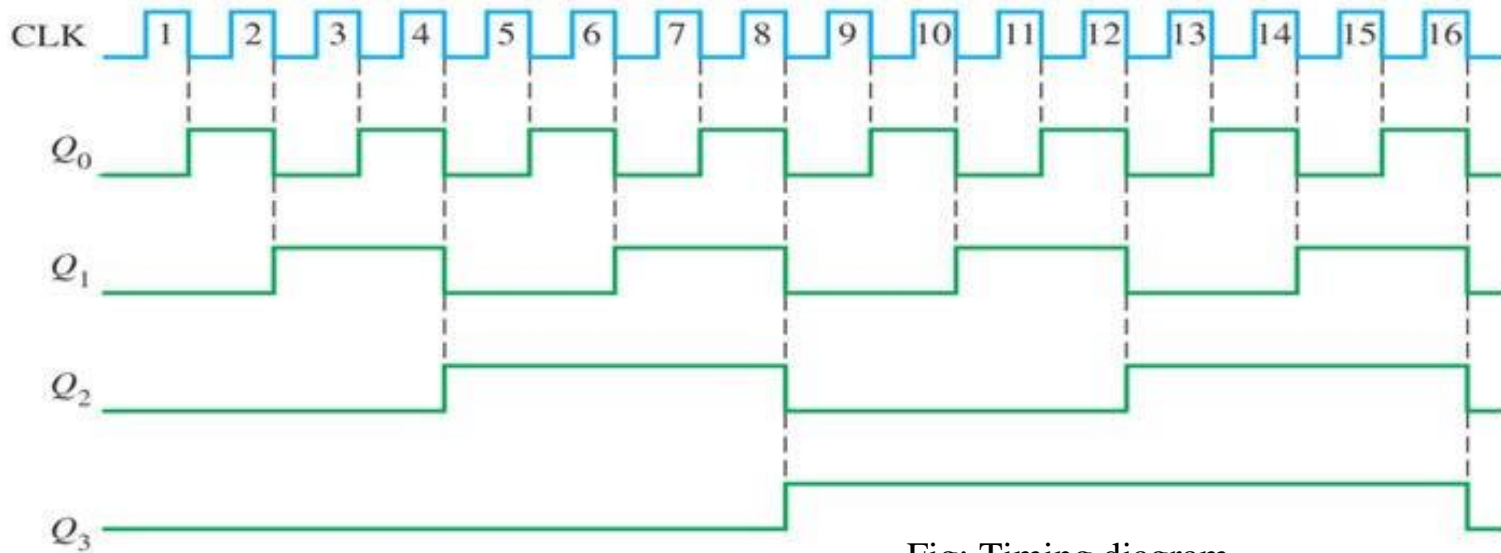


Fig: Timing diagram

BCD Ripple Counter (Decade Counter)

- These counters have 10 states in their sequence.
- A decade counter of states from 0000 to 1001 is called a **BCD decade counter**.
- Since the counter would have 16 states, it is forced to recycle before going through all of its possible state.
- The **BCD decade counter** is recycled to 0000 after the 1001 state.
- Such a counter must have at least four flip-flops to represent each decimal digit, since a decimal digit is represented by a binary code with at least four bits.
- The sequence of states in a decimal counter is dictated by the binary code used to represent a decimal digit.

 


Fig: state diagram

BCD Ripple Counter

| Q_3 | Q_4 | Q_2 | Q_1 |
|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 |

Fig: count sequence

 


FIGURE
BCD ripple counter

Operation:

- When CP input goes from 1 to 0, the flip-flop is set if $J = 1$, is cleared if $K = 1$, is complemented if $J = K = 1$, and is left unchanged if $J = K = 0$. The following are the conditions for each flip-flop state transition:
 1. Q_1 is complemented on the negative edge of every count pulse.
 2. Q_2 is complemented if $Q_8 = 0$ and Q_1 goes from 1 to 0. Q_2 is cleared if $Q_8 = 1$ and Q_1 goes from 1 to 0.
 3. Q_4 is complemented when Q_2 goes from 1 to 0.
 4. Q_8 is complemented when $Q_4 Q_2 = 11$ and Q_1 goes from 1 to 0. Q_8 is cleared if either Q_4 or Q_2 is 0 and Q_1 goes from 1 to 0.

 


Fig: Timing diagram

Ring Counter: Ring counter is a type of counter composed of flip-flops connected into a shift register, with the output of the last flip-flop fed to the input of the first, making a circular or ring structure.


 


Fig. 4-stage ring counter

count sequence of ring counter

| CLR/preset | CLK | Q ₀ | Q ₁ | Q ₂ | Q ₃ |
|------------|-----|----------------|----------------|----------------|----------------|
| 0 | X | 1 | 0 | 0 | 0 |
| 1 | ↓ | 0 | 1 | 0 | 0 |
| 1 | ↓ | 0 | 0 | 1 | 0 |
| 1 | ↓ | 0 | 0 | 0 | 1 |
| 1 | ↓ | 1 | 0 | 0 | 0 |

Timing diagram of ring counter.

 

Synchronous (Parallel) Counters

- Synchronous counters are distinguished from ripple counters in that **clock pulses are applied to the CP inputs of *all* flip-flops.**
- Synchronous counters are counters in which all the flip-flops are **triggered simultaneously (in parallel) by the clock input pulses.**
- All the FFs **change state simultaneously** in synchronization with the clock pulse.
- The decision whether a flip-flop is to be complemented or not is determined from the values of the J and K inputs at the time of the pulse.
 - If $J = K = 0$, the flip-flop remains unchanged. If $J = K = 1$, the flip flop complements.
- Synchronous counters have the **advantage of high speed but the disadvantage of having more circuitry** than that of asynchronous counters


Design of Synchronous Counter

- The design steps for synchronous sequential circuits can be summarized as:
 1. From the word description and specifications of the desired operation, derive a state diagram for the circuit.
 2. Obtain the State table
 3. Reduce the number of states if necessary.
 4. Assign binary values to the states.
 5. Determine the number of flip-flops needed and assign a letter symbol to each.
 6. Choose the type of flip-flops to be used
 7. From the state table, derive the circuit excitation and output tables.
 8. Derive the simplified flip-flop input equations and output equations.
 9. Draw the logic diagram.

Mod-5 Synchronous Counter

Page-1

Suppose we design using JK Flip Flop

 

State diagram

Determine the no. of flip flop needed

$$2^n \geq N$$

For Mod 5 $N=5$

$$\therefore 2^n \geq 5$$

$n=3$ i.e. 3 flip flop required.

Type of flip flop to be

used = JK flip flop (suppose)

Excitation Table for JK flip flop

| Q_n | Q_{n+1} | J | K |
|-------|-----------|---|---|
| 0 | 0 | 0 | X |
| 0 | 1 | 1 | X |
| 1 | 0 | X | 1 |
| 1 | 1 | X | 0 |

Transition Table

| Present state | | | Next state | | | | | | | | |
|---------------|-------|-------|------------|-------|-------|-------|-------|-------|-------|-------|-------|
| Q_C | Q_B | Q_A | Q_C | Q_B | Q_A | J_C | K_C | J_B | K_B | J_A | K_A |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | X | 0 | X | 1 | X |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | X | 1 | X | X | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | X | X | 0 | 1 | X |
| 0 | 1 | 1 | 1 | 0 | 0 | 1 | X | X | 1 | X | 1 |
| 1 | 0 | 0 | 0 | 0 | 0 | X | 1 | 0 | X | 0 | X |

K map simplification

For J_C

| $Q_B \backslash Q_A$ | 01 | 11 | 10 |
|----------------------|----|----|----|
| 00 | 0 | 1 | 0 |
| 10 | X | X | 0 |

$$\therefore J_C = Q_B Q_A$$

For K_C

| Q_C | $Q_B Q_A$ | 00 | 01 | 11 | 10 |
|-------|-----------|----|----|----|----|
| 0 | | X | X | X | X |
| 1 | | 1 | X | X | X |

$$K_C = 1$$

For J_B

| Q_C | $Q_B Q_A$ | 00 | 01 | 11 | 10 |
|-------|-----------|----|----|----|----|
| 0 | | 0 | 1 | X | X |
| 1 | | 0 | X | X | X |

$$J_B = Q_A$$

For K_B

| Q_C | $Q_B Q_A$ | 00 | 01 | 11 | 10 |
|-------|-----------|----|----|----|----|
| 0 | | X | X | 1 | 0 |
| 1 | | X | X | X | X |

$$K_B = Q_A$$

For J_A

| Q_C | $Q_B Q_A$ | 00 | 01 | 11 | 10 |
|-------|-----------|----|----|----|----|
| 0 | | 1 | X | X | 1 |
| 1 | | 0 | X | X | X |

$$J_A = \overline{Q_C}$$

For K_A

| Q_C | $Q_B Q_A$ | 00 | 01 | 11 | 10 |
|-------|-----------|----|----|----|----|
| 0 | | X | 1 | 1 | X |
| 1 | | X | X | X | X |

$$K_A = 1$$

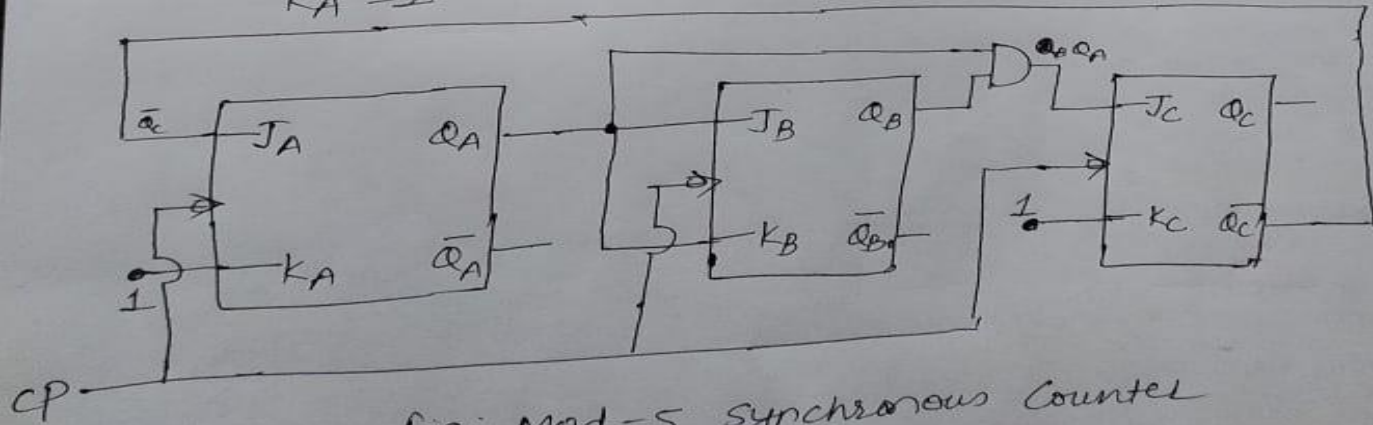


Fig: Mod-5 synchronous Counter Logic diagram.

Mod-7 Synchronous counter.
 → designed with J-K flip-flop.
 No. of flip-flop needed is


$$2^n \geq N$$

For Mod-7, $N = 7$

$$2^n \geq 7$$

$$n = 3$$

State diagram

 

Excitation table for JK flip-flop

| Q_n | Q_{n+1} | J | K |
|-------|-----------|---|---|
| 0 | 0 | 0 | X |
| 0 | 1 | 1 | X |
| 1 | 0 | X | 1 |
| 1 | 1 | X | 0 |

Transition table:

| present state | | | Next state | | | J_C K_C | | J_B K_B | | J_A K_A | |
|---------------|-------|-------|-------------|-------|-------|-------------|---|-------------|---|-------------|---|
| \bar{Q}_C | Q_B | Q_A | \bar{Q}_C | Q_B | Q_A | | | | | | |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | X | 0 | X | 1 | X |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | X | 1 | X | X | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | X | X | 0 | 1 | X |
| 0 | 1 | 1 | 1 | 0 | 0 | 1 | X | X | 1 | X | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | X | 0 | X | 0 | 1 | X |
| 1 | 0 | 1 | 1 | 1 | 0 | X | 0 | 1 | X | X | 1 |
| 1 | 1 | 0 | 0 | 0 | 0 | X | 1 | X | 1 | X | 0 |

K-Map Simplification:

K-Map for J_C

| | | | | |
|-------------|-----------------------|-----------------|-----------------|-----------|
| \bar{Q}_C | $\bar{Q}_B \bar{Q}_A$ | $\bar{Q}_B Q_A$ | $Q_B \bar{Q}_A$ | $Q_B Q_A$ |
| \bar{Q}_C | 0 | 0 | 1 | 0 |
| Q_C | X | X | X | X |

$$J_C = \bar{Q}_B Q_A$$

K-Map for K_C

| | | | | |
|-------------|-----------------------|-----------------|-----------------|-----------|
| \bar{Q}_C | $\bar{Q}_B \bar{Q}_A$ | $\bar{Q}_B Q_A$ | $Q_B \bar{Q}_A$ | $Q_B Q_A$ |
| \bar{Q}_C | X | X | X | X |
| Q_C | 0 | 0 | X | 1 |

$$K_C = \bar{Q}_B$$

K-Map for J_B

| | | | | |
|-------------|-----------------------|-----------------|-----------------|-----------|
| \bar{Q}_C | $\bar{Q}_B \bar{Q}_A$ | $\bar{Q}_B Q_A$ | $Q_B \bar{Q}_A$ | $Q_B Q_A$ |
| \bar{Q}_C | 0 | 1 | X | X |
| Q_C | X | 1 | X | X |

$$J_B = Q_A$$

K-Map for K_B

| | | | | |
|-------------|-----------------------|-----------------|-----------------|-----------|
| \bar{Q}_C | $\bar{Q}_B \bar{Q}_A$ | $\bar{Q}_B Q_A$ | $Q_B \bar{Q}_A$ | $Q_B Q_A$ |
| \bar{Q}_C | X | X | 1 | 0 |
| Q_C | 0 | X | X | 1 |

$$K_B = Q_A + Q_C Q_B$$

Map for J_A

| | | | | |
|-------------|-----------------------|-----------------|-----------------|-----------|
| | $\bar{Q}_B \bar{Q}_A$ | $\bar{Q}_B Q_A$ | $Q_B \bar{Q}_A$ | $Q_B Q_A$ |
| \bar{Q}_C | 1 | X | X | 1 |
| Q_C | 1 | X | X | X |

Map for K_A

| | | | | |
|-------------|-----------------------|-----------------|-----------------|-----------|
| | $\bar{Q}_B \bar{Q}_A$ | $\bar{Q}_B Q_A$ | $Q_B \bar{Q}_A$ | $Q_B Q_A$ |
| \bar{Q}_C | X | 1 | 1 | X |
| Q_C | X | 1 | X | 0 |

$$J_A = 1$$

$$K_A = Q_A$$

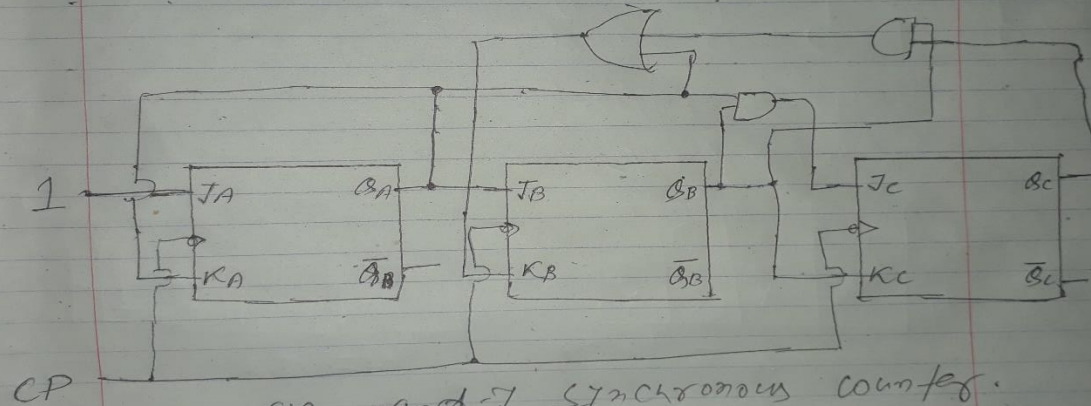


Fig. Mod-7 Synchronous counter.

Synchronous BCD Counter

- A BCD Counter is nothing but a **mod 10 counter**.
- It requires 4 FFs
- A BCD counter counts in binary-coded decimal from 0000 to 1001 and back to 0000 where states **0000 through 1001 are stable**.
- States 1010 through 1111 are invalid.
- After the tenth clock pulse, the counter resets.
- Because of the return to 0 after a count of 9, a BCD counter **does not have a regular pattern as in a straight binary count**.
- To derive the circuit of a BCD synchronous counter, it is necessary to go through a **design procedure** discussed earlier.

- The flip-flop input functions from the excitation table can be simplified by means of maps.
 - The unused states for minterms 10 to 15 are taken as don't-care terms.

Synchronous BCD Counter

| CLOCK PULSE | Q ₄ | Q ₃ | Q ₂ | Q ₁ |
|---------------|----------------|----------------|----------------|----------------|
| Initially | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 2 | 0 | 0 | 1 | 0 |
| 3 | 0 | 0 | 1 | 1 |
| 4 | 0 | 1 | 0 | 0 |
| 5 | 0 | 1 | 0 | 1 |
| 6 | 0 | 1 | 1 | 0 |
| 7 | 0 | 1 | 1 | 1 |
| 8 | 1 | 0 | 0 | 0 |
| 9 | 1 | 0 | 0 | 1 |
| 10 (recycles) | 0 | 0 | 0 | 0 |

Fig: count sequence

| Table Excitation requirements | | | | | | | | | | | | | | | |
|------------------------------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|---------------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| PS | | | | NS | | | | Required excitation | | | | | | | |
| Q ₄ | Q ₃ | Q ₂ | Q ₁ | Q ₄ | Q ₃ | Q ₂ | Q ₁ | J ₄ | K ₄ | J ₃ | K ₃ | J ₂ | K ₂ | J ₁ | K ₁ |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | X | 0 | X | 0 | X | 1 | X |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | X | 0 | X | 1 | X | X | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | X | 0 | X | X | 0 | 1 | X |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | X | 1 | X | X | 1 | X | 1 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | X | X | 0 | 0 | X | 1 | X |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | X | X | 0 | 1 | X | X | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | X | X | 0 | X | 0 | 1 | X |
| 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | X | X | 1 | X | 1 | X | 1 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | X | 0 | 0 | X | 0 | X | 1 | X |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | X | 1 | 0 | X | 0 | X | X | 1 |

| Q_2Q_1 | | | | | |
|----------|---|----|----|----|----|
| Q_4Q_3 | | 00 | 01 | 11 | 10 |
| | | | | | |
| 00 | | | | | |
| 01 | | | | 1 | |
| 11 | X | X | X | X | X |
| 10 | X | X | X | X | X |

$$J_4 = Q_3Q_2Q_1$$

| Q_2Q_1 | | | | | |
|----------|---|----|----|----|----|
| Q_4Q_3 | | 00 | 01 | 11 | 10 |
| | | | | | |
| 00 | X | X | X | X | X |
| 01 | X | X | X | X | X |
| 11 | X | X | X | X | X |
| 10 | | 1 | X | X | X |

$$K_4 = Q_1$$

| Q_2Q_1 | | | | | |
|----------|---|----|----|----|----|
| Q_4Q_3 | | 00 | 01 | 11 | 10 |
| | | | | | |
| 00 | | | | 1 | |
| 01 | X | X | X | X | X |
| 11 | X | X | X | X | X |
| 10 | | | X | X | X |

$$J_3 = Q_2Q_1$$

| Q_2Q_1 | | | | | |
|----------|---|----|----|----|----|
| Q_4Q_3 | | 00 | 01 | 11 | 10 |
| | | | | | |
| 00 | | | 1 | X | X |
| 01 | | | 1 | X | X |
| 11 | X | X | X | X | X |
| 10 | | | | X | X |

$$J_2 = \bar{Q}_4Q_1$$

| Q_2Q_1 | | | | | |
|----------|---|----|----|----|----|
| Q_4Q_3 | | 00 | 01 | 11 | 10 |
| | | | | | |
| 00 | X | X | 1 | | |
| 01 | X | X | 1 | | |
| 11 | X | X | X | X | X |
| 10 | X | X | X | X | X |

$$K_2 = Q_1$$

| Q_2Q_1 | | | | | |
|----------|---|----|----|----|----|
| Q_4Q_3 | | 00 | 01 | 11 | 10 |
| | | | | | |
| 00 | X | X | X | X | X |
| 01 | | | | 1 | |
| 11 | X | X | X | X | X |
| 10 | X | X | X | X | X |

$$K_3 = Q_2Q_1$$

Fig. K-maps for excitations of the BCD counter using J-K flip-flops


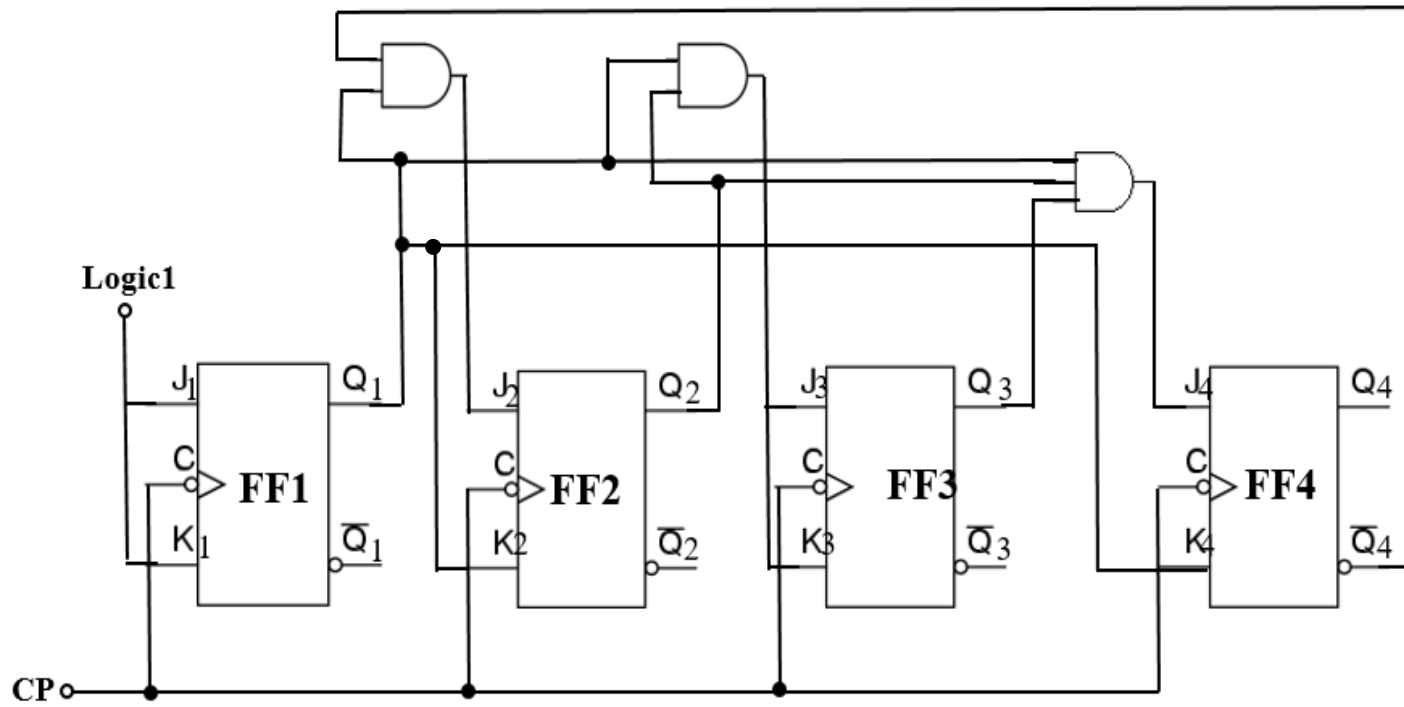


Fig: Logic Diagram

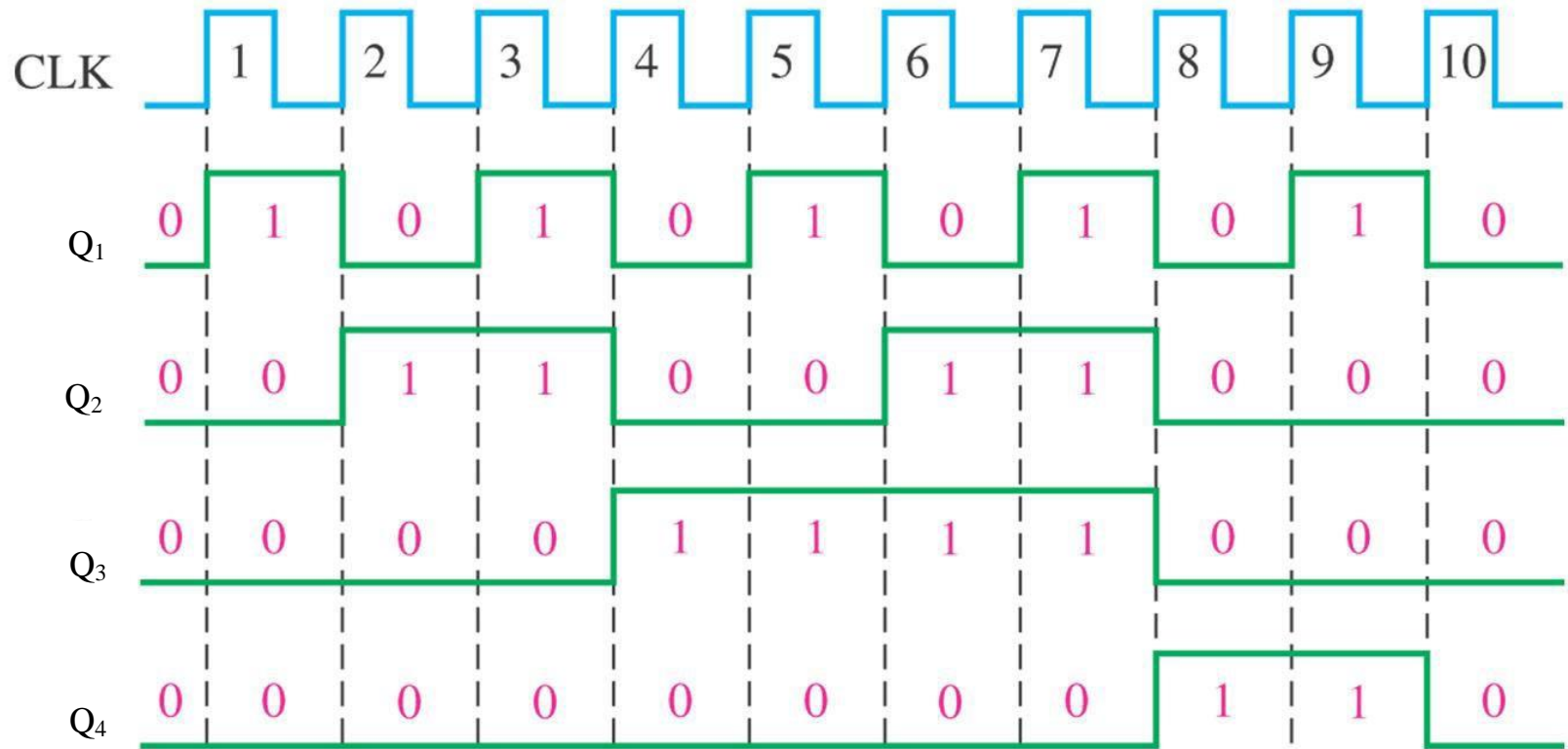


Timing diagram for the BCD decade counter (Q₀ is the LSB).


Mod 6 Counter

| PS | | | NS | | | Required excitation | | | | | |
|-------|-------|-------|-------|-------|-------|---------------------|-------|-------|-------|-------|-------|
| Q_3 | Q_2 | Q_1 | Q_3 | Q_2 | Q_1 | J_3 | K_3 | J_2 | K_2 | J_1 | K_1 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | X | 0 | X | 1 | X |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | X | 1 | X | X | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | X | X | 0 | 1 | X |
| 0 | 1 | 1 | 1 | 0 | 0 | 1 | X | X | 1 | X | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | X | 0 | 0 | X | 1 | X |
| 1 | 0 | 1 | 0 | 0 | 0 | X | 1 | 0 | X | X | 1 |


(a) Excitation table

Mod 6 Counter

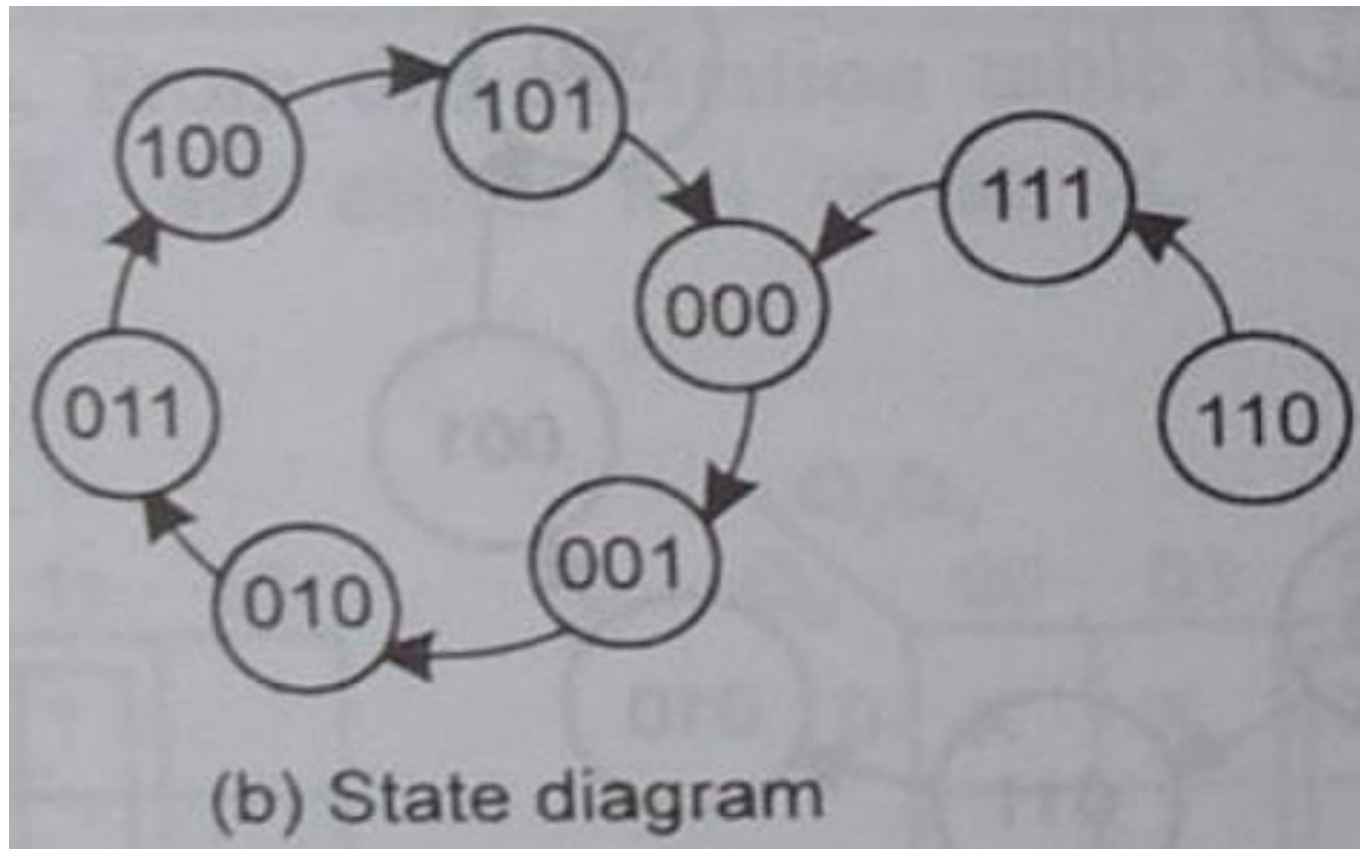


 


$$J_3 = Q_2Q_1$$

 


$$K_3 = Q_1$$

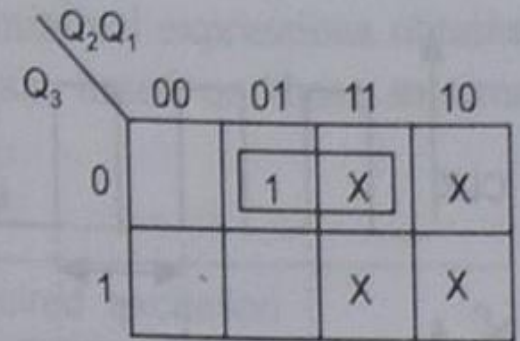


$$J_2 = \bar{Q}_3Q_1$$

 

$$K_2 = Q_1$$

 

$$J_1 = 1$$

 

$$K_1 = 1$$

Fig. K-maps for excitations of synchronous mod-6 counter using J-K flip-flops

4-bit asynchronous down counter:

⇒ 4-bit ⇒ 4 flip-flops

No. of states, $N = 2^n$


$n = 4$, $N = 2^4 = 16$ states

Maximum count = $16 - 1 = 15$


In down count maximum count comes first, i.e. 15 to 0.

Used JK flip-flop
positive edge triggered flip-flop

Logic 1

 

Timing diagram:

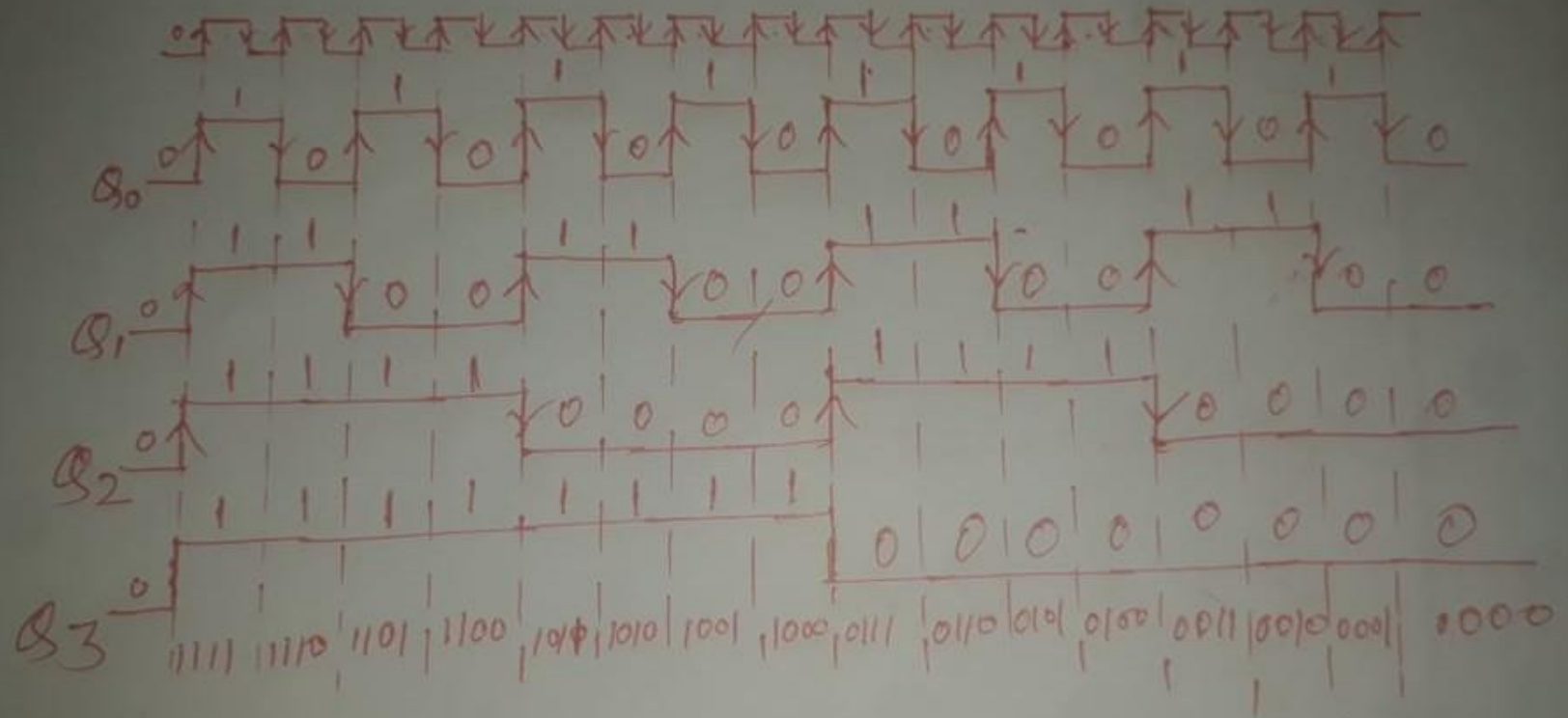

3-bit UP-DOWN Ripple Counter:

In this type of counter both up and down modes are combined.

A mode control input (M) is used to ~~set~~ select counting.

Using mode control input M:

$M = 0 \rightarrow$ UP counting


$M = 1 \rightarrow$ DOWN counting

- In case of ripple counter, when we connect output of Q_0 to clock input of FF1, it starts up counting.
- When we connect output of \bar{Q}_0 to clock input of FF1, it starts down counting.

So, we have to develop combinational logic circuit to use $M = 0$ for up counting and $M = 1$ for down counting.

3-bit UP-down Ripple Counter

Block diagram

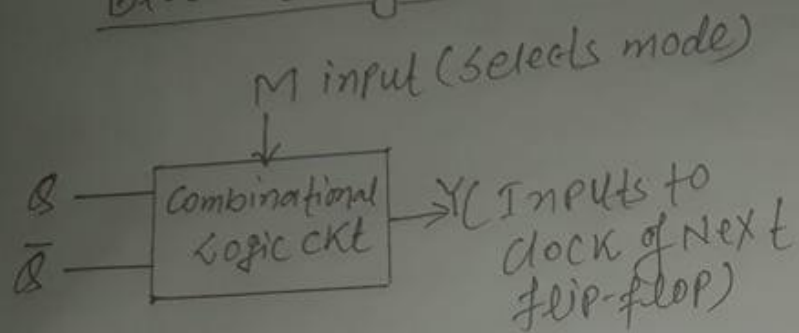

K-map

| M \ Q \bar{Q} | | | | |
|-----------------|----|----|----|----|
| | 00 | 01 | 10 | 11 |
| 0 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 |

Truth table for above ckt


| Inputs | | | output Y | |
|---------------|---|-----------|-------------|------------------------------------|
| M | Q | \bar{Q} | | |
| UP Counting | 0 | 0 | 0 | UP Counting depends on Q |
| | 0 | 0 | 1 | |
| | 0 | 1 | 1 | |
| | 0 | 1 | 1 | |
| Down Counting | 1 | 0 | 0 | Down Counting depends on \bar{Q} |
| | 1 | 0 | 1 | |
| | 1 | 1 | 0 | |
| | 1 | 1 | 1 | |
| | 1 | 1 | 1 | |

$$\therefore Y = \bar{M}Q + M\bar{Q}$$

Johnson Counter or Twisted Ring Counter

In Johnson Counter, the ~~output~~ complemented output (i.e. \bar{Q}) of last flip-flop is fed to the input of first flip-flop. So, it is called twisted ring counter.

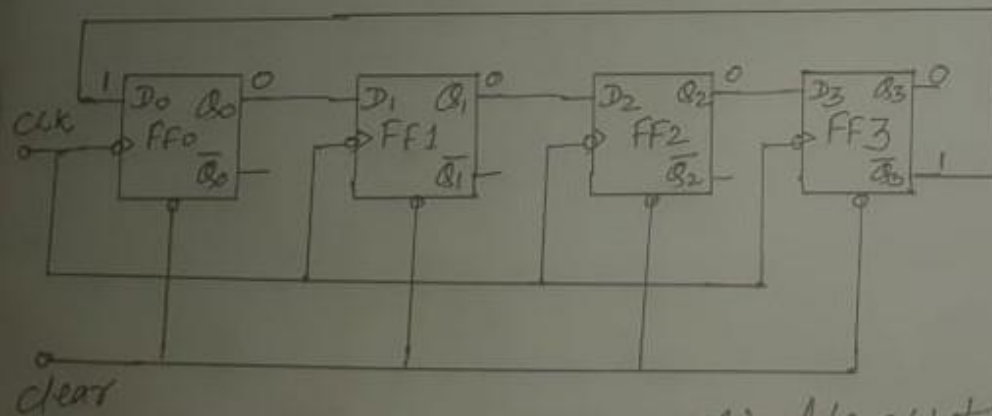- Reset input is not required
- Number of states = $2 \times \text{number of flip-flop}$



Note: Clear and Preset is overriding inputs. When we activate these inputs, only clear and preset works. Clear and preset are active low inputs.

Initially clear input is applied to all the FFs i.e. $\text{clear} = 0$. So O/P of all the FFs are 0 initially.


Johnson Counter

Count sequence table

| CLR | CLOCK | Q ₀ | Q ₁ | Q ₂ | Q ₃ |
|-----|-------|----------------|----------------|----------------|----------------|
| 0 | X | 0 | 0 | 0 | 0 |
| 1 | ↓ | 1 | 0 | 0 | 0 |
| 1 | ↓ | 1 | 1 | 0 | 0 |
| 1 | ↓ | 1 | 1 | 1 | 0 |
| 1 | ↓ | 1 | 1 | 1 | 1 |
| 1 | ↓ | 0 | 1 | 1 | 1 |
| 1 | ↓ | 0 | 0 | 1 | 1 |
| 1 | ↓ | 0 | 0 | 0 | 1 |
| 1 | ↓ | 0 | 0 | 0 | 0 |

→ Q₃ = 1, then $\bar{Q}_3 = 0$

Timing diagram

 


3-bit synchronous down counter

$$2^3 = 8 = 7 \text{ to } 0$$

We use three negative edge triggered FFs.

| Q2 | Q1 | Q0 | J2 | K2 | J1 | K1 | J0 | K0 |
|----|----|----|----|----|----|----|----|----|
| 1 | 1 | 1 | x | 0 | x | 0 | x | 1 |
| 1 | 1 | 0 | x | 0 | x | 1 | 1 | x |
| 1 | 0 | 1 | x | 0 | 0 | x | x | 1 |
| 1 | 0 | 0 | x | 1 | 1 | x | 1 | x |
| 0 | 1 | 1 | 0 | x | x | 0 | x | 1 |
| 0 | 1 | 0 | x | x | x | 1 | 1 | x |
| 0 | 0 | 1 | 0 | x | 0 | x | x | 1 |
| 0 | 0 | 0 | 1 | x | 1 | x | 1 | x |

K-map for J2, K2, J1, K1, J0, K0

 

3-bit synchronous Up-down counter:

Number of flip-flops used= 3

Total number of Counts = $2^3 = 8$

For up-counting 0-7 and for down counting 7-0


Clock pulse is simultaneously given to all the flip-flops.

A mode control input (M) is used to select counting.

M = 0 up counting

M = 1 down counting


State diagram:

 

Truth table 3-bit Up down Counter:

| Control Input M | Present State Q ₃ Q ₂ Q ₁ | | | Next State Q ₃ Q ₂ Q ₁ | | | FFs Inputs T ₃ T ₂ T ₁ | | |
|--------------------|---|---|---|--|---|---|--|---|---|
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 |

K-Map for T_3

 

$$T_3 = M Q_2' Q_1' + M' Q_2 Q_1$$

Introduction to Registers


- An *n -bit register* has a group of n flip-flops and some logic gates and is capable of storing n bits of information.
 - The *flip-flops store the information* while the gates control when and how new information is transferred into the register.

Some functions of register:

- ❖ retrieve data from register
- ❖ store/load new data into register (serial or parallel)
- ❖ shift the data within register (left or right)

Introduction to Registers

 - No external gates.
- **Example: A 4-bit register.** A new 4-bit data is loaded every
- clock cycle.



Registers with Parallel Load

- Instead of loading the register at every clock pulse, we may **want to control when to load**.
- *Loading* a register: transfer new information into the register. Requires a *load* control input.
- *Parallel loading*: all bits are loaded simultaneously.

Shift Registers


- Another function of a register, besides storage, is to provide for *data movements*.
- Each *stage* (flip-flop) in a shift register represents one bit of storage, and the shifting capability of a register permits the movement of data from stage to stage within the register, or into or out of the register **upon application of clock pulses**.
- A register capable of shifting its binary information either to the right or to the left is called a **shift register**.

- The logical configuration of a shift register consists of a chain of flip-flops connected in cascade, with the **output of one flip-flop connected to the input of the next flip-flop**.
- All flip-flops receive a common clock pulse that causes the shift from one stage to the next.

Shift Registers

- Generally, shift registers operate in one of four different modes with the basic movement of data through a shift register being:
- **Serial-in to Parallel-out (SIPO)** - the register is loaded with serial data, one bit at a time, with the stored data being available in parallel form.
- **Serial-in to Serial-out (SISO)** - the data is shifted serially "IN" and "OUT" of the register, one bit at a time in either a left or right direction under clock control.

 - **Parallel-in to Serial-out (PISO)** - the parallel data is loaded into the register simultaneously and is shifted out of the register serially one bit at a time under clock control.
- **Parallel-in to parallel-out (PIPO)**
 - the parallel data is loaded simultaneously into the register, and transferred together to their respective outputs by the same clock pulse.



Serial-in to Parallel-out (SIPO) Shift Register

- Accepts data **serially**.
- Outputs of **all stages are available simultaneously**.

 


Fig: Block diagram of 4-bit SIPO Shift register


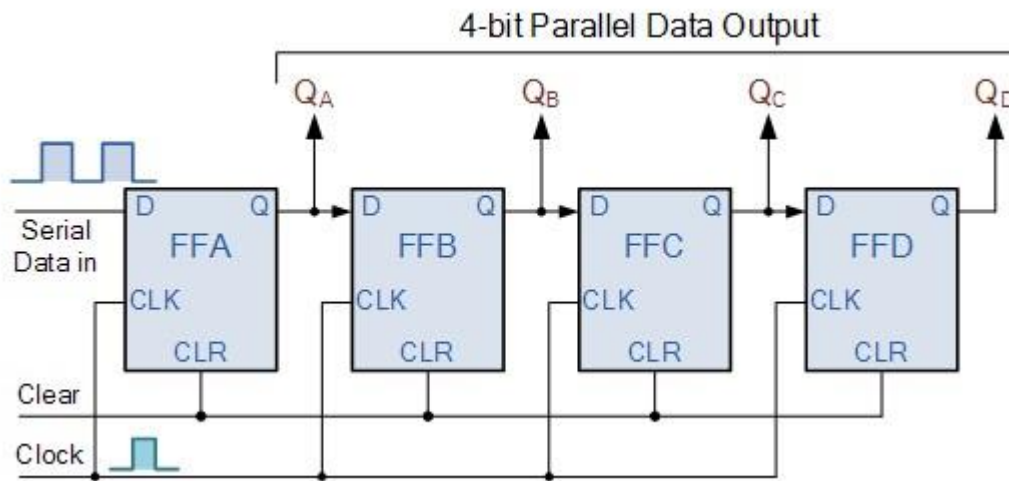


Fig. 4 bit serial
in parallel out
shift register

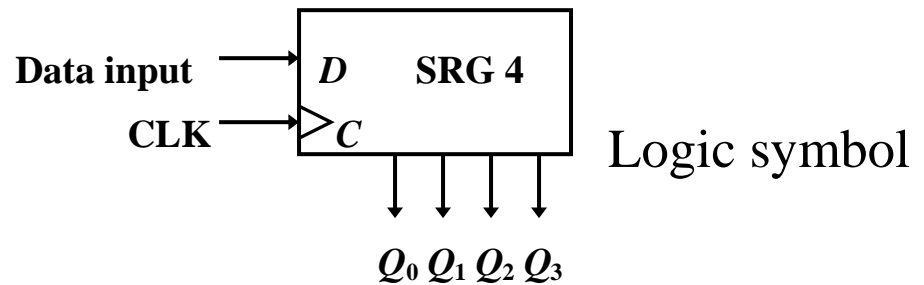


- Let us assume that all the flip-flops (FFA to FFD) have just been RESET (CLEAR input) and that all the outputs Q_A to Q_D are at logic level “0” i.e., no parallel data output.
- If a logic “1” is connected to the DATA input pin of FFA then on the first clock pulse the output of FFA and therefore the resulting Q_A will be set

HIGH to logic “1” with all the other outputs still remaining LOW at logic “0”.

- Assume now that the DATA input pin of FFA has returned LOW again to logic “0” giving us one data pulse or 0-1-0.
- The second clock pulse will change the output of FFA to logic “0” and the output of FFB and Q_B HIGH to logic “1” as its input D has the logic “1” level on it from Q_A .
- When the third clock pulse arrives this logic “1” value moves to the output of FFC (Q_C) and so on until the arrival of the fifth clock pulse which sets all the outputs Q_A to Q_D back again to logic level “0” because the input to FFA has remained constant at logic level “0”.
- The effect of each clock pulse is to shift the data contents of each stage one place to the right, and this is shown in the following table until the data value of 0-0-0-1 is

| Clock Pulse No | QA | QB | QC | QD |
|----------------|----|----|----|----|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 2 | 0 | 1 | 0 | 0 |
| 3 | 0 | 0 | 1 | 0 |
| 4 | 0 | 0 | 0 | 1 |
| 5 | 0 | 0 | 0 | 0 |

Shifting data 10000 serially

 

Timing diagram

Serial In/Serial Out Shift Registers

- Accepts data **serially** – **one bit at a time** – and also produces **output serially**.

Shifting data 1011


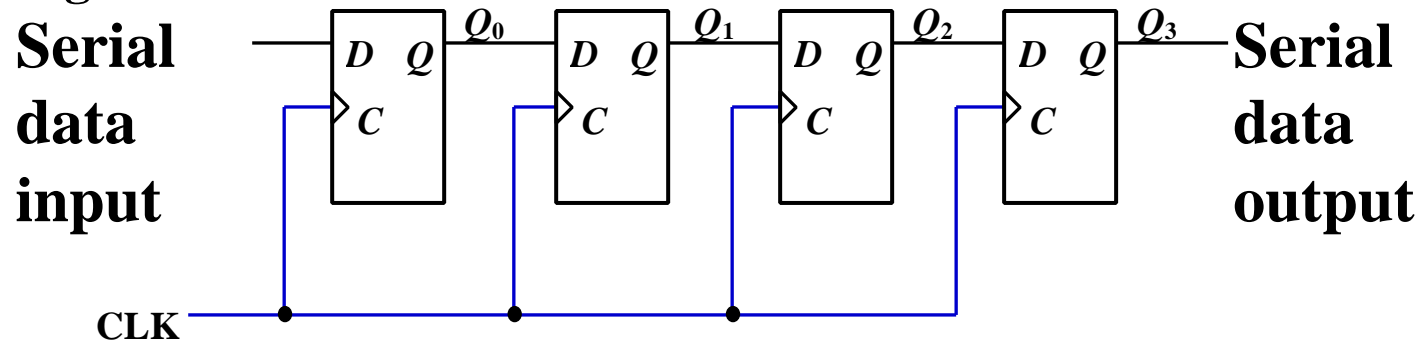


Fig: Serial in serial out shift register logic diagram

- This **shift register** is very similar to the SIPO except the data was read directly in a parallel form from the outputs Q_A to Q_D in SIPO, but the **data is allowed to flow straight** through the register and data out in the other end.
- Since there is only one output, the **DATA leaves the shift register one bit at a time in a serial pattern**, hence the name **Serial-in to Serial-Out Shift Register** or **SISO**.


| Clock Pulse Number | Q_0 | Q_1 | Q_2 | Q_3 |
|--------------------|-------|-------|-------|-------|
| Initially | 0 | 0 | 0 | 0 |
| ↑ | 1 | 0 | 0 | 0 |
| ↑ | 1 | 1 | 0 | 0 |
| ↑ | 0 | 1 | 1 | 0 |
| ↑ | 1 | 0 | 1 | 1 |

Timing diagram of SISO Shift Register

 

Parallel In/Serial Out Shift Registers

- Bits are entered **simultaneously, but output is serial.**
- The data is loaded into the register in a parallel in which all the data bits enter their inputs simultaneously, to the parallel input pins P_A to P_D of the register.
- The data is read out sequentially in the normal shift-right mode from the register at Q representing the data present at P_A to P_D .
- It is important to note that in this type of shift register **a clock pulse is not required to parallel load the register** as it is already present, but **four clock pulses are required to unload the data.**

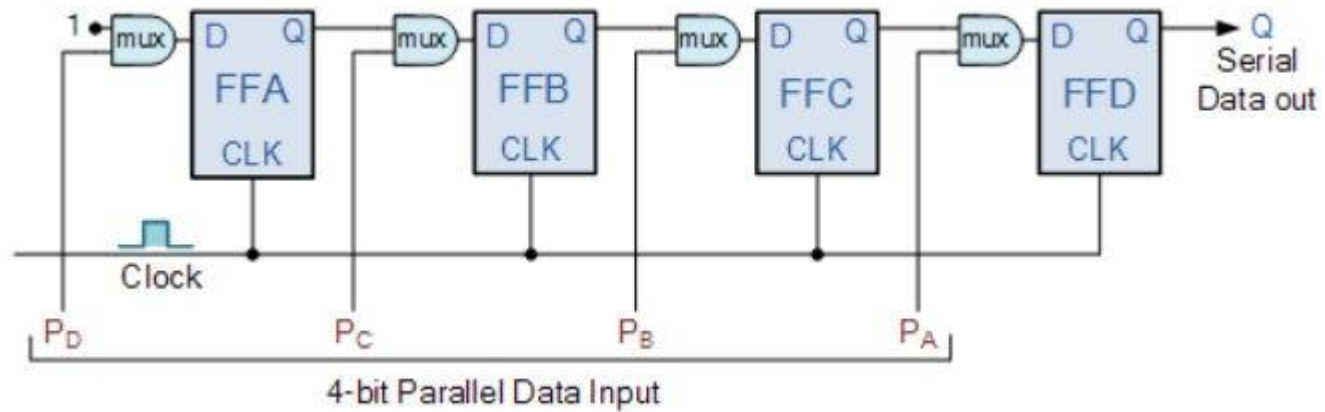


Data loaded

| DA | DB | DC | DE |
|----|----|----|----|
| 1 | 1 | 0 | 1 |

Data Shifted

| Clock pulse | QA | QB | QC | QD (Data output) |
|-------------|----|----|----|------------------|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 |
| 2 | 0 | 1 | 1 | 0 |
| 3 | 0 | 0 | 1 | 1 |
| 4 | 0 | 0 | 0 | 1 |

Timing diagram

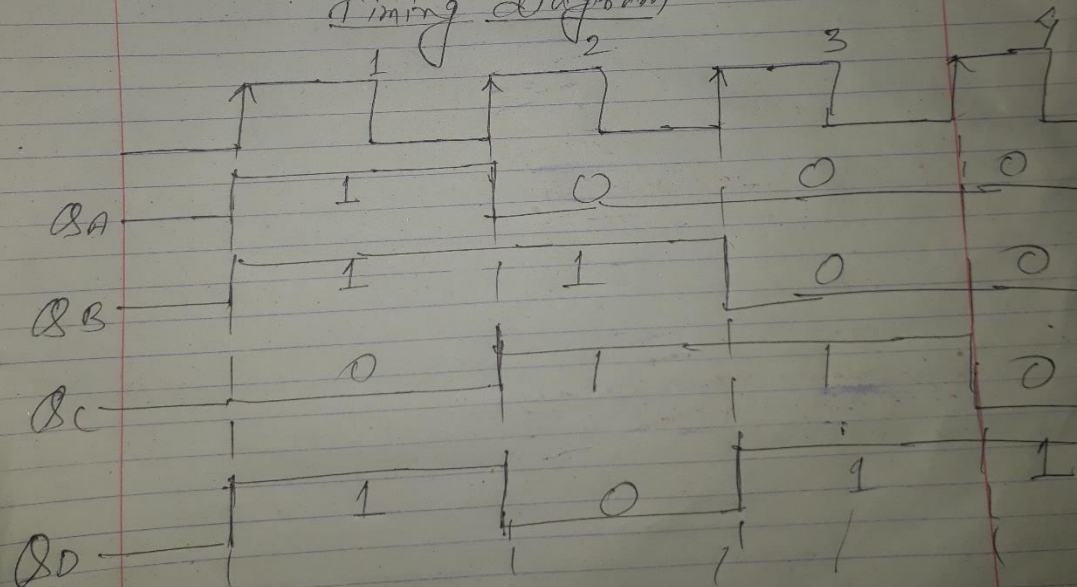

Parallel In/Parallel Out Shift Registers

- Simultaneous input and output of all data bits.
- The data is presented in a parallel format to the parallel input pins P_A to P_D and then transferred together directly to their respective output pins Q_A to Q_D by the same clock pulse.

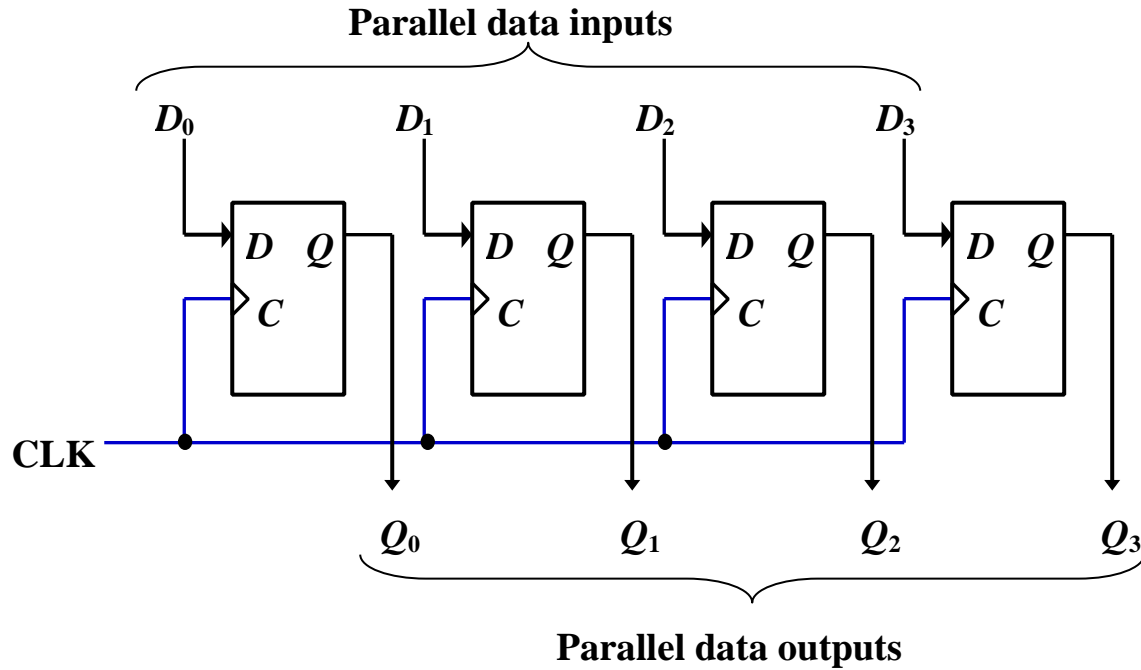


Fig: parallel in parallel out shift register logic diagram

1011

