 


TRIBHUVAN UNIVERSITY

# PATAN MULTIPLE CAMPUS

PATAN DHOKA, LALITPUR



DIGITAL LOGIC (BIT 103)

LAB ..8..

SUBMITTED BY

NAME: Suresh Dahal


CLASS: BIT-II

ROLL NO: 23

DATE: 2080/12/16

SUBMITTED TO

JYOTI PRAKASH CHAUDHARY

.....  
  
CHECKED BY

TITLE:- REALIZE THE FLIP-FLOP CIRCUITS WITH LOGIC DIAGRAM, CHARACTERISTIC TABLE AND LOGIC FUNCTION.

i) Clocked SR FLIP-FLOP

a) OBJECTIVE

→ To realize SR flip-flop circuit with characteristic table, logic diagram and logic function

b) REQUIREMENT

i) Digital logic kit and simulator

ii) 2 AND gates, 1 clock input, 2 NOR gates

iii) Connecting wires

iv) Interactive sequence generator as input


v) LED as output

c) THEORY

1. INTRODUCTION

SR flip-flop has two inputs R and S and two outputs i.e. normal and complemented. It has two states set and reset. It should be given a clock pulse to change its state otherwise it doesn't change value regardless of inputs variation.

2. LOGIC DIAGRAM

 

### 3. CHARACTERISTIC TABLE

$Q$	$S$	$R$	$Q(t+1)$
0	0	0	0 NC
0	0	1	0 Reset
0	1	0	1 set
0	1	1	Invalid cond <sup>n</sup>
1	0	0	1 NC
1	0	1	0 Reset
1	1	0	1 set
1	1	1	Invalid cond <sup>n</sup>

$S$	$R$	$Clock$	$Q(t+1)$	Comments
0	0	X	$Q$	NC
0	1	↑	0	Reset
1	0	↑	1	set
1	1	↑	?	Invalid

### 4. CHARACTERISTIC EQUATION

$Q$	$\overline{SR}$	$\overline{SR}$	$SR$	$SR$
$\overline{Q}$			X	1
$Q$	1		X	1

$$Q(t+1) = S + R'Q$$

### 1) CONCLUSION

In this lab, we have realized the clocked RS flip-flop circuit with logic diagram, characteristic table and logic function.

## ii) JK FLIP-FLOP

### a) OBJECTIVE

→ To realize the JK flip flop with logic diagram, characteristic table and logic function

### b) REQUIREMENT


- i) Digital Logic kit and simulator
- ii) 2 AND gates, 2 OR gates
- iii) Connecting wires
- iv) Interactive / sequence generator as input
- v) LED as output

### c) THEORY

#### 1. INTRODUCTION

JK is a refinement of the RS flip-flop to resolve invalid condition in RS flipflop. In JK, output  $Q$  is ANDed with  $K$  and  $CP$  inputs so that the flip-flop is cleared during a clock pulse only if  $Q$  was previously 1. Similarly  $Q'$  is ANDed with  $J$  and  $CP$  inputs.

#### 2. LOGIC DIAGRAM

 


### 3. CHARACTERISTIC TABLE

Q	J	K	Q(t+1)
0	0	0	0 NC
0	0	1	0 Reset
0	1	0	1 set
0	1	1	1 toggle
1	0	0	1 NC
1	0	1	0 Reset
1	1	0	1 set
1	1	1	0 toggle

J	K	Q(t+1)
0	0	Q NC
0	1	0 Reset
1	0	1 set
1	1	Q' toggle

### 4. CHARACTERISTIC EQUATION

 

$$Q(t+1) = JQ' + K'Q$$

### d) CONCLUSION :-

In this Lab, we have realized JK flipflop with logic diagram, characteristics table and equation.



### iii) D-FLIP-FLOP

#### a) OBJECTIVE

→ To realize the D flip-flop circuit with logic circuit, characteristics table and logic expression.

#### b) REQUIREMENT


- i) Digital logic kit and simulator
- ii) 1 NOT gate, 4 NAND gates
- iii) Connecting wires
- iv) Interactive / sequence generator as input
- v) LED as output

#### c.) THEORY

##### 1. INTRODUCTION:-

D flip flop means delay flip flop. It delays the output and gives input as output. It has only one input D.

##### 2. LOGIC DIAGRAM:-

 

##### 3. CHARACTERISTIC TABLE

Q	D	Q+1
0	0	0
0	1	1
1	0	0
1	1	1

Inputs		Outputs	
clk	D	Q	$\bar{Q}$
0	X	NC	NC
1	0	0	1
1	1	1	0

#### 4. CHARACTERISTIC EQUATION

Q	D	
	$\bar{D}$	D
$\bar{Q}$		1
Q		1

$$Q(t+1) = D$$

#### 1) CONCLUSION:-

In this lab, we have realized the D-flip-flop circuit with logic diagram, characteristics table and characteristics equation.

#### iv) T-FLIP-FLOP

#### a) OBJECTIVE

→ To realize T flip-flop with logic diagram, characteristics table and equation

#### b) REQUIREMENT

i) Digital logic kit or simulator

ii) 2 AND gates, 2 NOR gates

iii) Connecting wires

iv) Interactive / sequence generator as input


v) LED as output

## 1.) THEORY

### 1. INTRODUCTION

T means toggle flip-flop. It is a single input version of JK flip-flop. Regardless of present state, the flip-flop complements its state when clock pulse occurs while input T is 1.

### 2. LOGIC DIAGRAM

 

### 3. CHARACTERISTICS TABLE

Q	T	Q <sub>t+1</sub>
0	0	0
0	1	1
1	0	1
1	1	0

T	Q <sub>t+1</sub>
0	Q <sub>t</sub> No change
1	$\bar{Q}_t$ Complement

### 4. CHARACTERISTIC EQUATION

Q	T	$\bar{T}$	T
0			
0			1
1	1		

$$Q(t+1) = T \cdot \bar{Q} + \bar{T} \cdot Q$$

### d) CONCLUSION:-

In this Lab, we have realized T-flip-flop with logic diagram, characteristic table and characteristic equation.